

Assignment 9 (GATE, EC 2017-16)

Manasa

December 2020

0.1 QUESTION

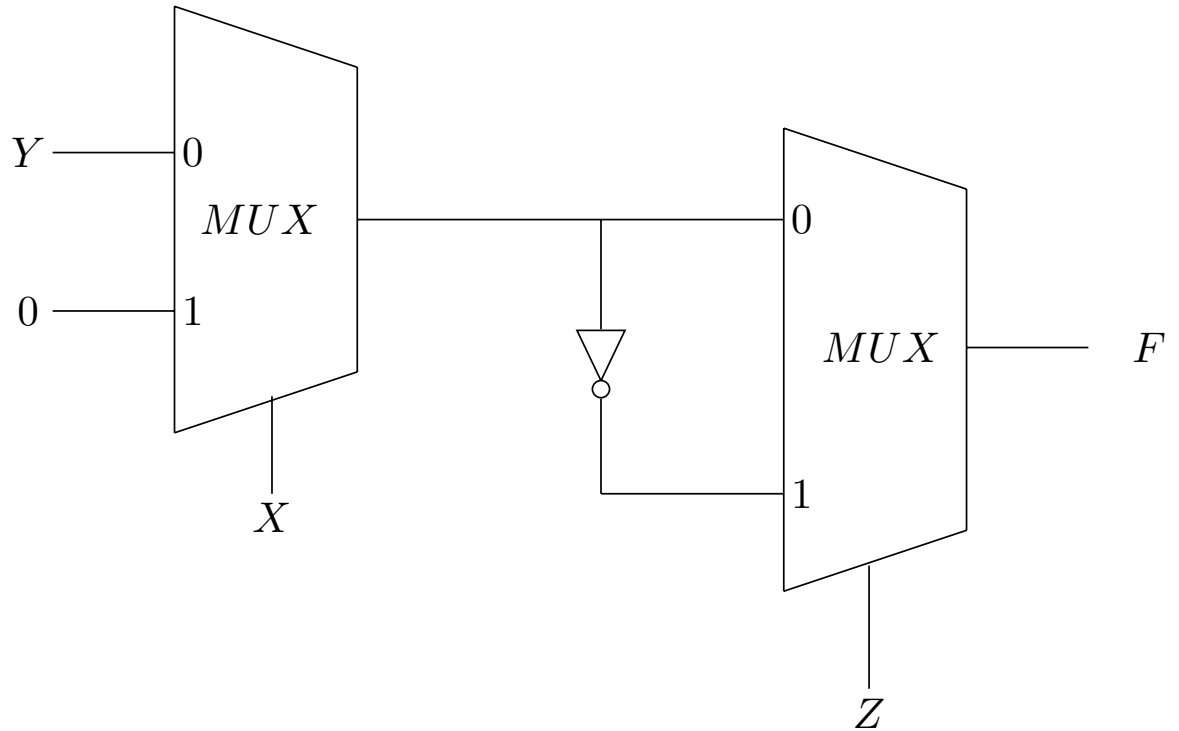


Figure 1:

Consider the circuit shown in the figure. The Boolean expression F implemented by the circuit is

1. $X'Y'Z' + XY + Y'Z$
2. $X'YZ' + XZ + Y'Z$
3. $X'YZ' + XY + Y'Z$

$$4. X'Y'Z' + XZ + Y'Z$$

0.2 SOLUTION

From figure 1,

In first multiplexer the input signals are Y and 0, control line is X. According to this the output signal is $X'Y$

In second multiplexer the input signals are $X'Y$ and $(X'Y)'$ control line is Z. The output signal is F.

$$F = X'YZ' + ((X'Y)')Z$$

$$= X'YZ' + (X + Y')Z \quad (\text{Using demorgan laws})$$

$$= X'YZ' + XZ + Y'Z$$

So the boolean expression F implemented by the circuit is

$$F = X'Y Z' + XZ + Y'Z \quad (1)$$

0.3 CIRCUIT

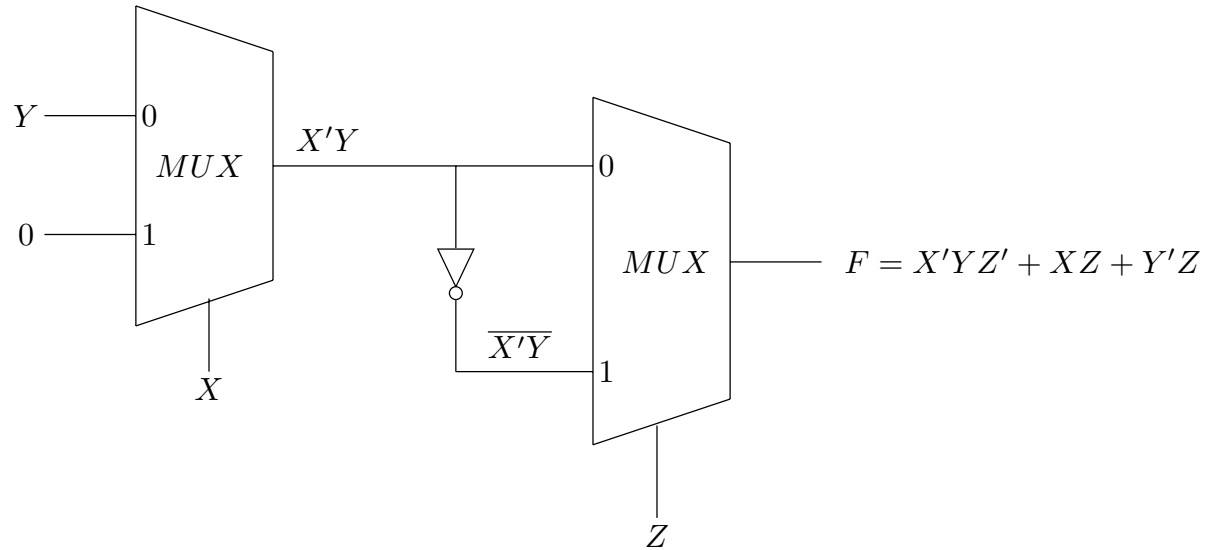


Figure 2:

From the above figure we can derive the expression of F

$$F = X'YZ' + XZ + Y'Z \quad (2)$$

| X | Y | Z | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

0.4 TRUTH TABLE of Expression F